

---

# Line Follower Robot

---

Robotics Workshop  
Currents 15<sup>th</sup> march 2008  
EEE Department  
NIT Trichy

---

**Developed By:**  
Mayur Agarwal  
Prashant Agrawal  
Krishna Nand Gupta  
Hitesh Meghani

---

## To Our Readers

We are glad to have had an opportunity to share our knowledge with interested robotics enthusiasts. In this book we have attempted to provide a brief compilation of our experiences in robotics (participating and winning in Technical Festivals all over the country), extending over last three years.

The prospect of practically implementing engineering concepts is the hallmark of robotics. By reading the basics in this book you will gain a significant insight into various tools employed in shaping a robot. However to participate in technical festivals with ever changing problem statements you will be required to apply these basics concepts and come up with innovative algorithms and superior designs.

Do not expect this book to be a panacea for all robotic problems, rather you will have to sit and work for hours to get a functioning robot. Transform each failure into a stepping stone instead of stumbling over it. We appreciate the beauty of diamond but little do we wonder how it became so bright? Its perseverance extending thousands of years transformed it into its present sparkling state.

We encourage you to plunge further into the field of robotics with dedicated perseverance, make your own mistakes and gain valuable experience from them.

ALL THE BEST

Your valuable suggestions and inquisitive doubts are welcome. You can contact us at

Mayur Agarwal ([mayurmagic.nitt@gmail.com](mailto:mayurmagic.nitt@gmail.com))

Krishna Nand Gupta ([kng\\_sweet94@yahoo.com](mailto:kng_sweet94@yahoo.com))

Prashant Agarwal ([pras\\_nitt@yahoo.co.in](mailto:pras_nitt@yahoo.co.in))

Hitesh Meghani ([h.nittian@gmail.com](mailto:h.nittian@gmail.com))

# Introduction

The line follower is a self operating robot that detects and follows a line that is drawn on the floor. The path consists of a black line on a white surface (*or vice versa*). The control system used must sense a line and maneuver the robot to stay on course, while constantly correcting the wrong moves using feedback mechanism, thus forming a simple yet effective closed loop System. The robot is designed to follow very tight curves.

## Sample Paths

The path is a black line on a white background with width of 3 cm (except at bends where a little variation may be present). It may contain paths laterally displaced by around 3 cm and also gap of at most 5 cm. (*All these specifications may vary from one competition to another*).

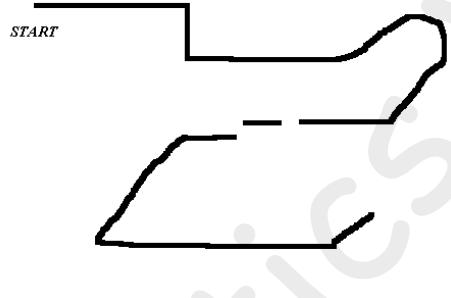


Figure 1: Basic Sample Arena

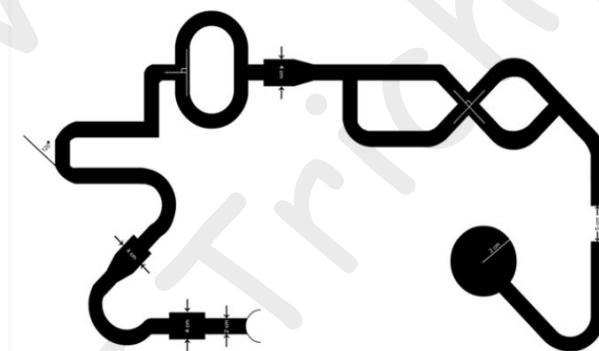


Figure 2: Sample Arena of Kurukshetra'08 (Anna University)

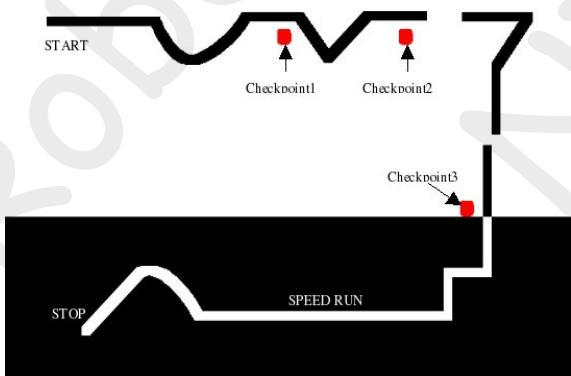


Figure 3: Sample Arena of Pragyan'07 (NIT Trichy)

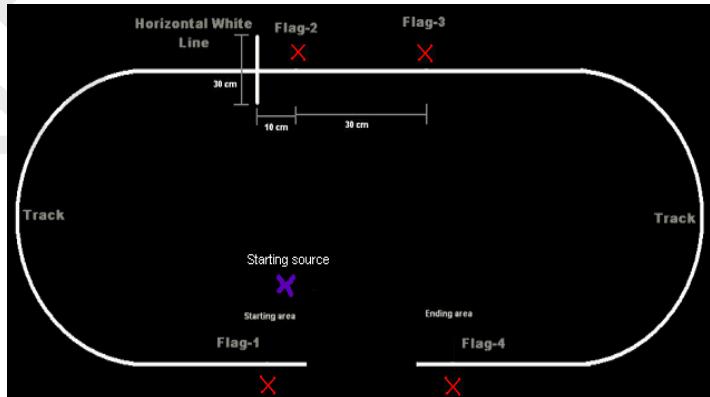


Figure 4: Sample Arena of Robo-Relay of Kishitii'08 (IIT KGP)

*From above images we can conclude that in most of line follower competitions, some additional task has to be performed apart from following the line.*

# Basic design and requirements


The robot is built using ATmega8L, L293D, IR sensors, LM324, platform consisting of a toy car chassis (or hand made Aluminum sheet chassis), two motors and controlling wheels. It has infrared sensors on the bottom for detecting black tracking tape. Line position is captured with the help of these optical sensors called opto-couplers mounted at the front end of the robot. (*Each opto-coupler consists of an IR LED and an IR Sensor*). When the sensors detect black surface, output of comparator, LM324 is low, while for white surface the output is high. It is sent as input to the microcontroller for accurate control and steering of motors. Microcontroller ATmega8L and Motor driver L293D are used to drive the motors.

## Basic operation

The basic operations of the line follower are as follows:

1. Capture line position with optical sensors mounted at front end of the robot. For this a combination of IR LED and Photo Transistor called an opto-coupler is used. The line sensing process requires high resolution and high robustness.
2. Steer robot to track the line with a suitable steering mechanism. To achieve this we use two motors that govern the motion of the wheels on either side.

## Block Diagram

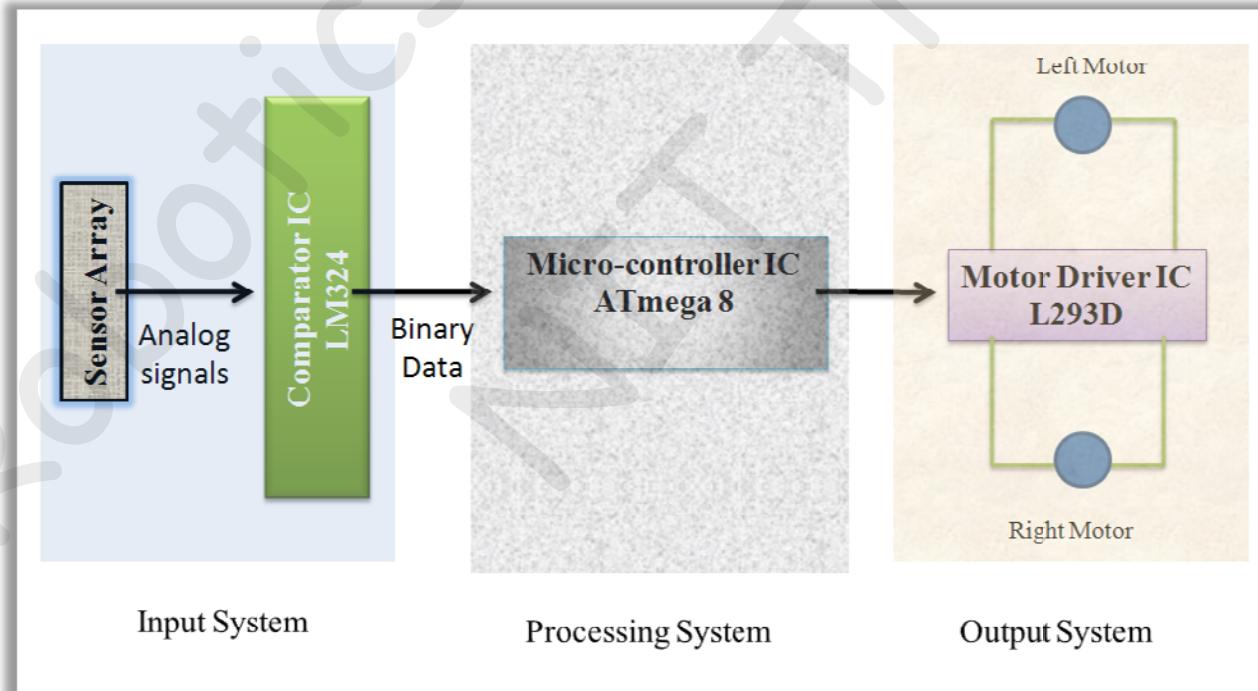

Let's see all the system in detail.

# INPUT SYSTEM

## Sensors

Each opto-coupler has one emitter (IR LED) and one receiver (Photo-Transistor or photo diode).

If white surface is present beneath the IR LED, IR rays are reflected and are sensed by the receiver, while in case of black surface, the light gets absorbed and hence receiver does not sense IR rays.


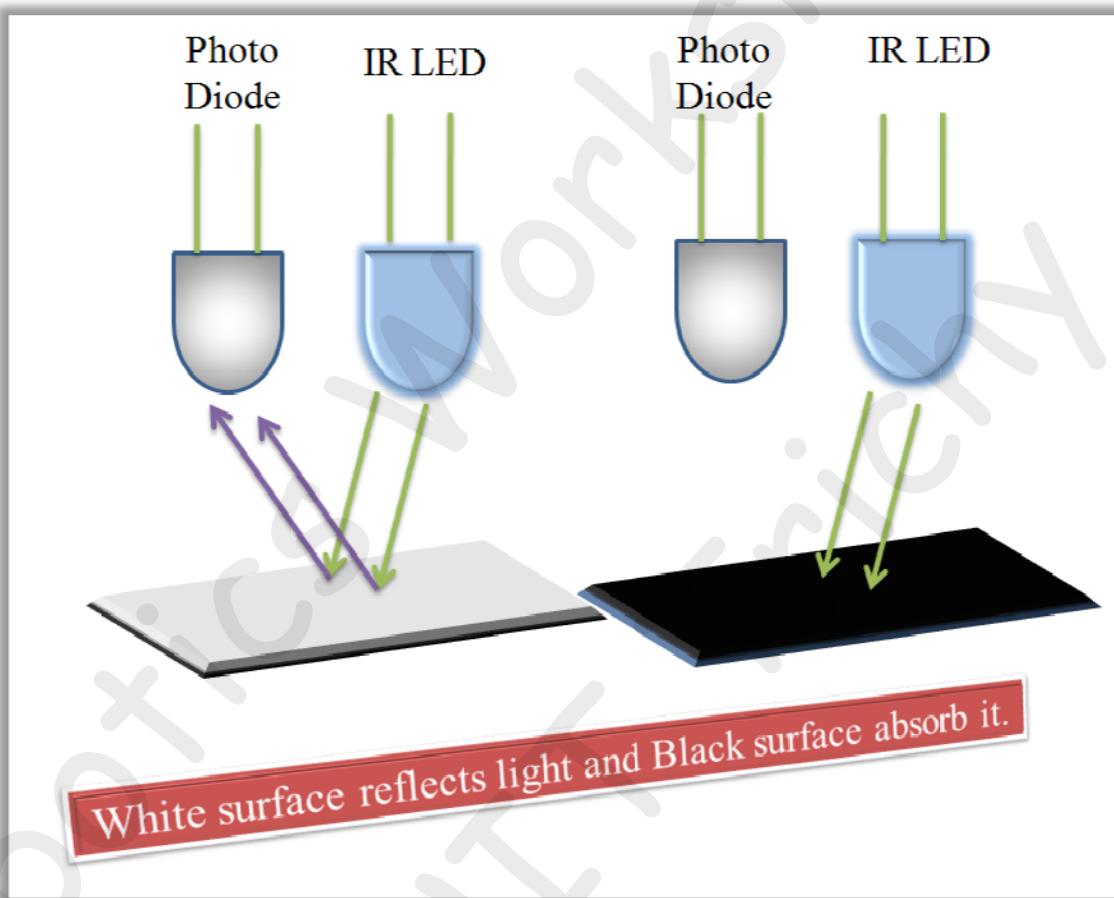



Photo diode has a property that if IR light falls on it, its electrical resistance decreases (from say  $150\text{k}\Omega$  to  $10\text{k}\Omega$ ). For sensing the change in resistance we use voltage divider circuit (as shown in figure below).

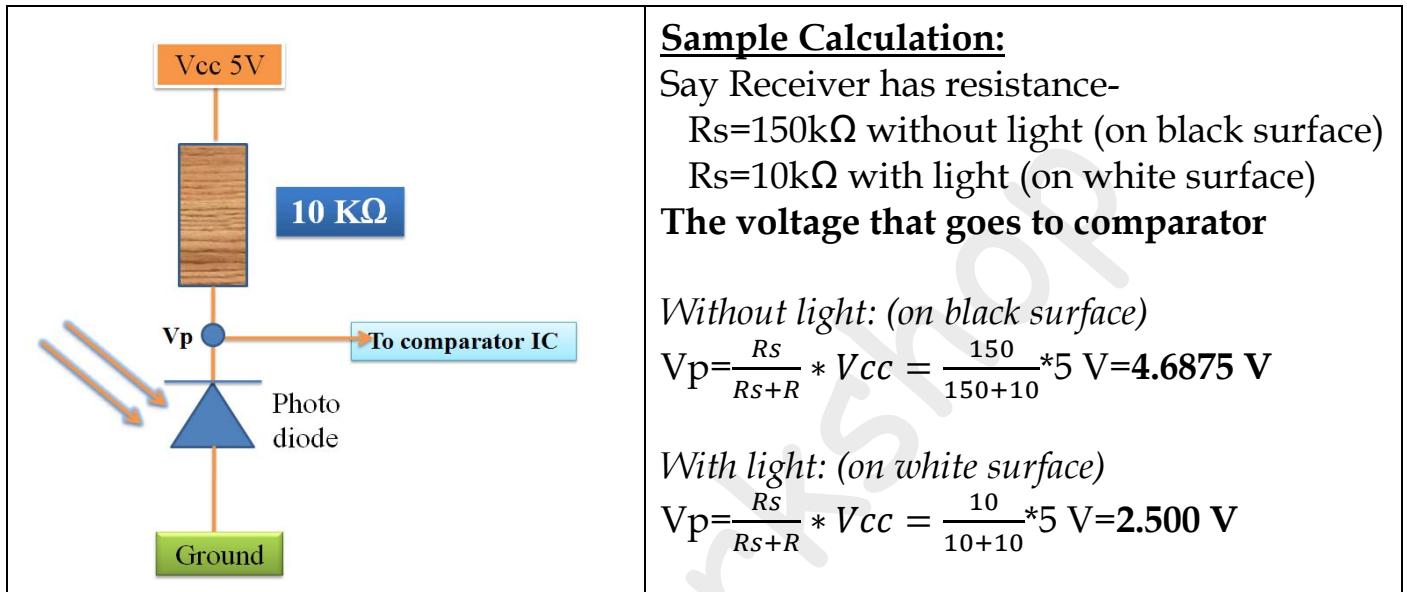


Thus we get the variation in voltage, which is sensed by the comparator IC (LM324). The comparator then, gives logical high or low according to input.
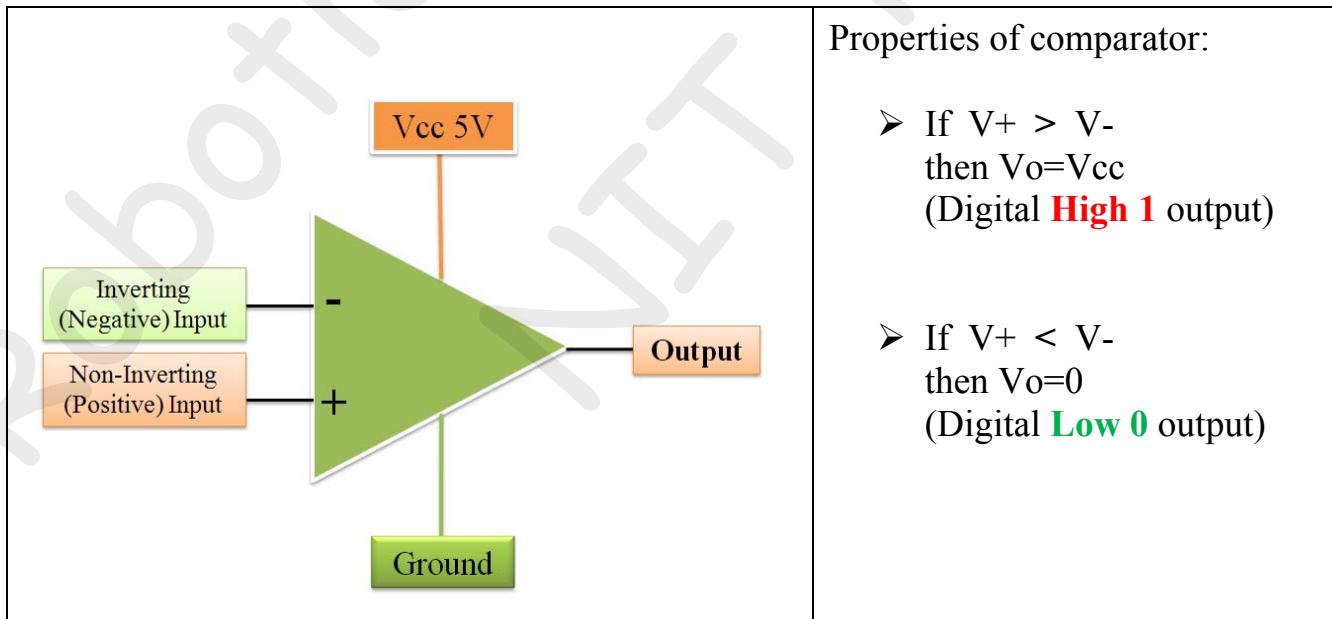
## Comparator

Comparator is a device which compares two input voltages and gives output as high or low. In a circuit diagram it is normally represented by a triangle having-Inverting (negative) Input (-), Non-Inverting (positive) Input(+), Vcc, Ground, Output.



Let's see some examples

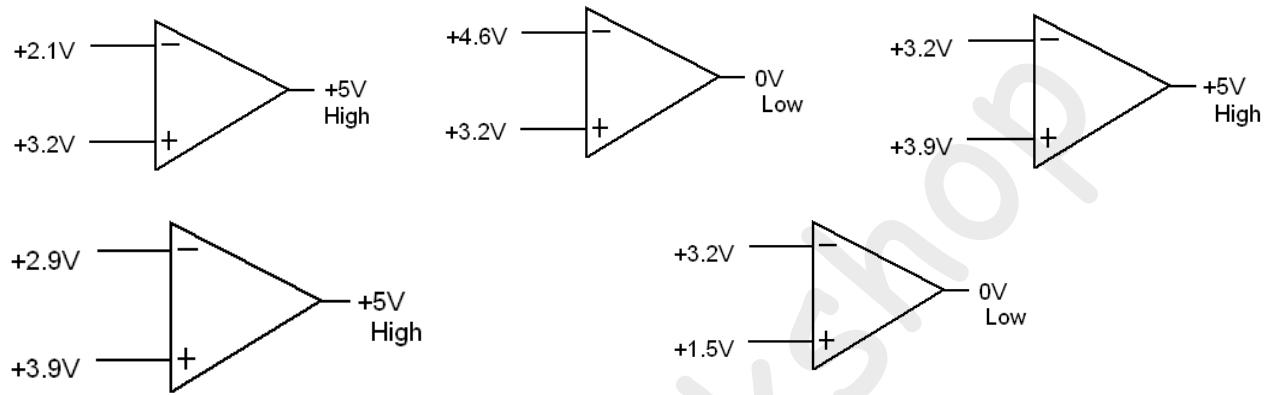

## Use of comparator in IR sensor


As above we see that two inputs are required for comparator. One input is from photo-receiver (like photo-diode), other is generated by us using potentiometer (*preset*). The second voltage is also called as reference voltage for that sensor.

## Setting of reference voltage (Vref)

We can vary reference voltage by using potentiometer, such that it can vary from 0V to Vcc. We set the reference voltage as mean value of the sensor outputs measured with and without light.

$$\text{From above example } V_{ref} = \frac{4.675 + 2.500}{2} = 3.5875 \text{ V}$$

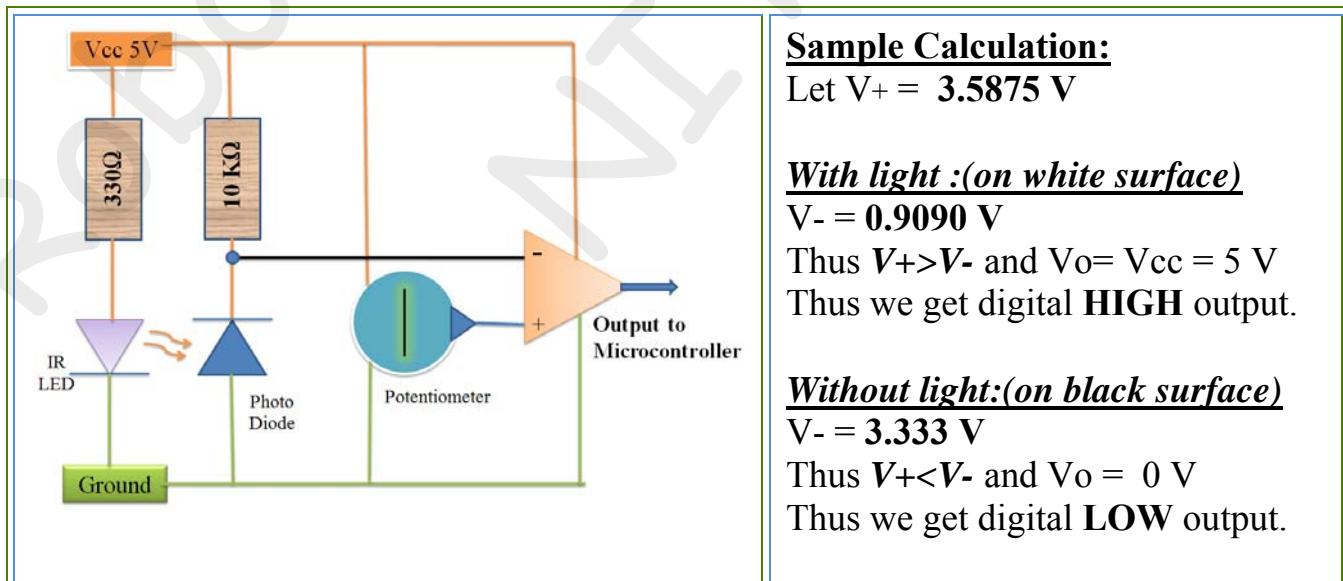
Lets connect Inverting Input of Comparator to photo- receiver, Non-Inverting Input to potentiometer (as shown in figure) and output to micro controller.



*Note: If we connect Inverting Input of Comparator to potentiometer (preset) and Non-Inverting Input to photo- receiver, the only difference observed is that at white surface we get Low output and for black surface we get High output.*

## IC LM324

IC LM324 contains four comparators.

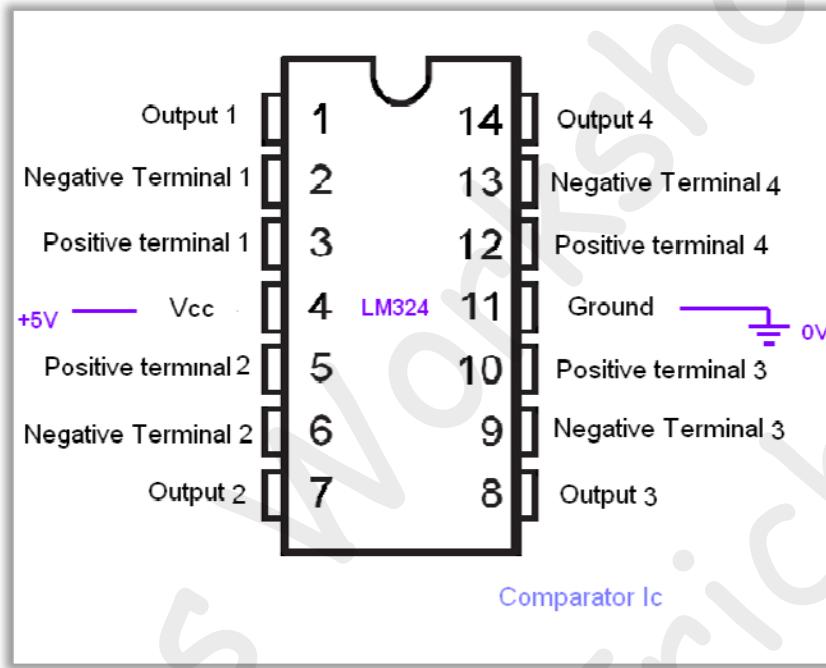

You can see the datasheet of IC LM324 for more details.

## Arrangement of Sensors


An array of sensors arranged in a straight row pattern is bolted under the front of the robot. It is used to locate the position of line below the robot.

We can use any **number of sensors**. If we have lesser number of sensors then the robot movement will not be smooth and it may face problems at sharp turns. If we use higher number of sensors robot movement will become smooth and reliable for sharp turns, however it requires complex programming and more hardware. Thus we must choose optimum number of sensors.

The **distance between sensors** depends on

1. Number of sensors used
2. Width of straight line
3. Distance between sensors may not be constant (it depends on the logic).

Sample figure:

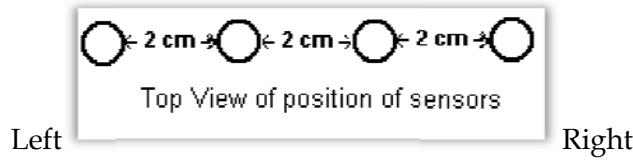

## Tips for Input System

- Significant problems are faced in input system. So to make reliable connections use PCB.
- Set preset value for each sensor, because each sensor may behave differently and may give different voltage on the same surface.
- You have to adjust preset value for new surface, as reflectivity depends on roughness of surface.
- The advantage of IR sensor is that it is less affected by ambient light. In case we use LDR as photo detector, its sensitivity will highly depend on ambient light.
- To get a good voltage swing, the value of R1 must be carefully chosen, we generally use  $10k\Omega$  resistance.
- Proper orientation of the IR LED and Photo diode is must so as to have good voltage swing. Also IR rays of one opto-coupler should not disturb the other opto-coupler.
- If an opto-coupler is not working then first check whether the voltage across IR LED is 1.1-1.2 V, then check the voltage variation across the photo diode for black and white surfaces, then set the reference voltage.

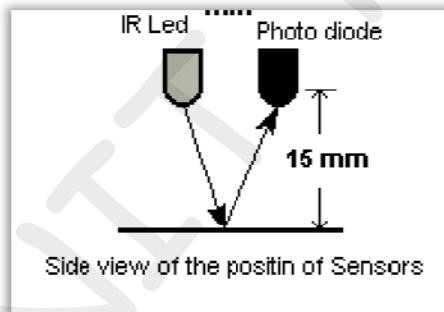


Figure 2: Alignment of Sensor in an opto-coupler

# Voltage Regulator 78xx

Voltage regulators convert fixed DC output voltage from variable DC. The most commonly used ones are 7805 and 7812. 7805 gives fixed 5V DC voltage if input voltage is in between 7.5V to 20V.

They help to maintain a steady voltage level despite varying current demands and input voltage variations.

If input voltage is <7.5 V then regulation won't be proper i.e. if input is 6V then output may be 5V or 4.8V, but there are some parameters for the voltage regulators like maximum output current capability, line regulation etc., that won't be proper.

To identify the leads of the 7805, you have to keep the lead downward (Fig a) and the writing to your side, (see the figure below). You can see the heat sink above the voltage regulator.(1-input,2-gnd,3-output).



Fig a


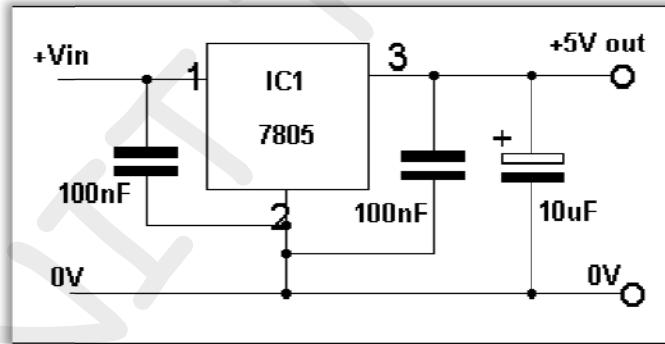


Fig b

Fig b shows how to use 7805 voltage regulator. Here you can see that coupling capacitors are used for good regulation. But there is no need for it in normal case. But if 7805 is used in analog circuit we should use capacitor, otherwise the noise in the output voltage will be high. The mainly available 78xx IC's are 7805, 7809, 7812, 7815, 7824.
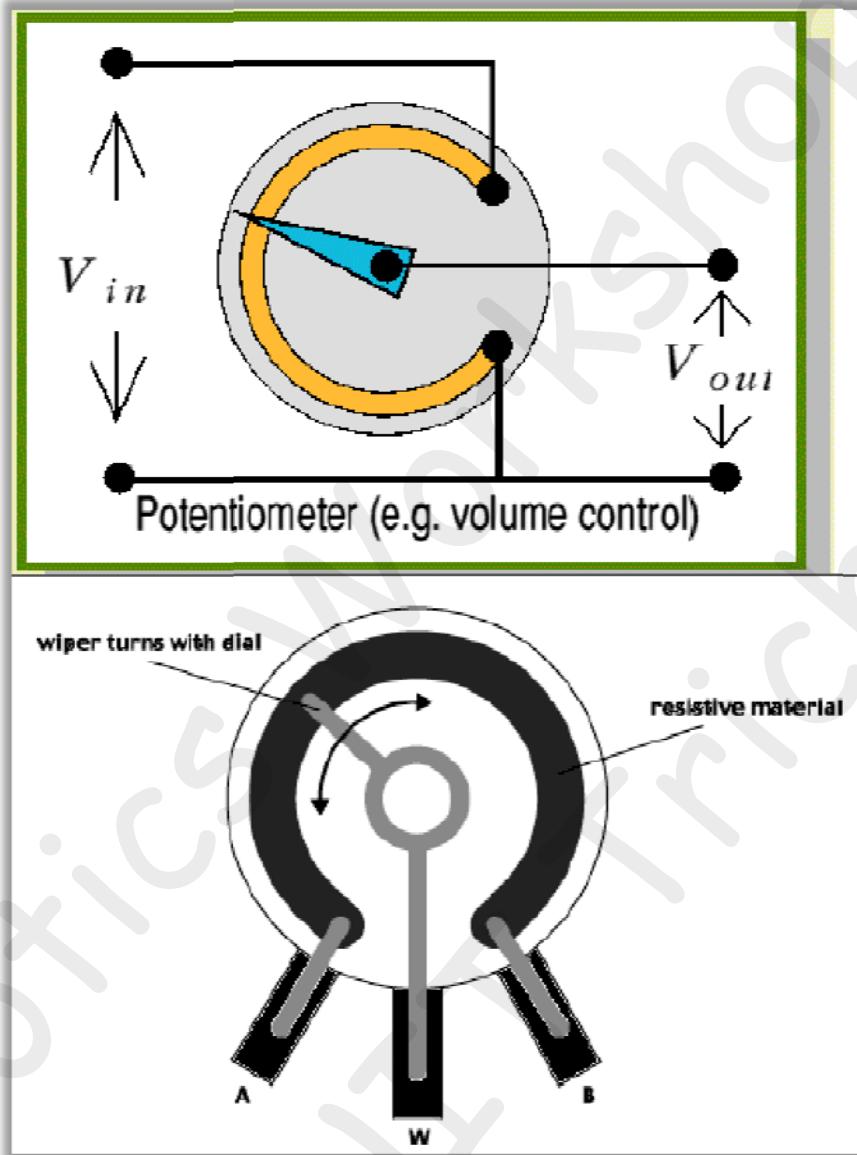
# POTENTIOMETER ('POT')



Potentiometer is a variable resistor which is used to vary the resistance by rotating the shaft. Potentiometers are available from 100 ohm to 470Kohm (or more).



Potentiometer is a voltage divider. If we connect Lead A to Vcc and Lead B to ground then you can get voltages from 0 to Vcc by at Lead W. Mainly potentiometers are used to generate reference voltage for LM324.

*Note: To reduce the value of current drawn, use the presets that have higher overall resistance.*

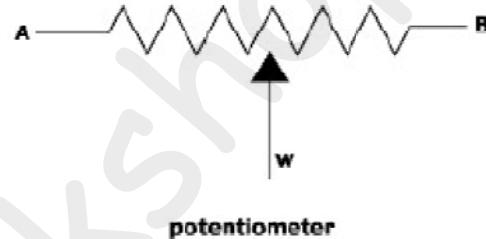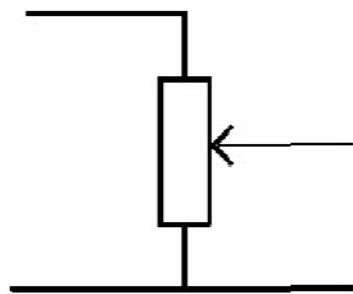**Standard circuit symbol  
for a potentiometer**



Above figure shows different types of potentiometers available. Second and third potentiometers are mainly used when you only want to change the value of resistance occasionally while the first one is used when we have to vary resistance frequently. Second and third ones are easy to insert in breadboard and PCB, also they remain fixed. They are also called **Preset**. Resistance is varied by rotating the shaft in the body of the potentiometer.

# PROCESSING SYSTEM

Processing system acts as the **Brain** of robot, which generates desired output for corresponding inputs. For that we use microcontrollers. In present days, there are several companies that manufacture microcontrollers, for example **ATMEL**, **Microchip**, **Intel**, **Motorola** etc. We will be using **ATmega8L** microcontroller in our robot. It is an ATMEL product. It is also called **AVR**.

## Why ATmega8L

Line follower robot requires simple microcontroller as it uses simple algorithms. We can use any microcontroller for that. But we use ATmega8L, because it has following extra features:

1. It is an **ISP (In System Programmable)** device. It means programming (Burning) of ATmega8L IC can be done without removing it from the system.  
*Note: Programming (Burning) of a microcontroller means transferring the code from computer to microcontroller .Burning is explained later.*
2. It has on chip **PWM (Pulse Width Modulation)** circuit at three pins (Pin 15, 16 and 17). We have explained PWM in appendix section.
3. It has an inbuilt RC **oscillator**. (Oscillator is a clock generator circuit).
4. It consumes lesser power than other microcontrollers.

## A) Hardware Details

(RESET) PC6	1	28	□ PC5 (ADC5/SCL)
(RXD) PD0	2	27	□ PC4 (ADC4/SDA)
(TXD) PD1	3	26	□ PC3 (ADC3)
(INT0) PD2	4	25	□ PC2 (ADC2)
(INT1) PD3	5	24	□ PC1 (ADC1)
(XCK/T0) PD4	6	23	□ PC0 (ADC0)
VCC	7	22	□ GND
GND	8	21	□ AREF
(XTAL1/TOSC1) PB6	9	20	□ AVCC
(XTAL2/TOSC2) PB7	10	19	□ PB5 (SCK)
(T1) PD5	11	18	□ PB4 (MISO)
(AIN0) PD6	12	17	□ PB3 (MOSI/OC2)
(AIN1) PD7	13	16	□ PB2 (SS/OC1B)
(ICP1) PB0	14	15	□ PB1 (OC1A)

# Basic hardware connections of ATmega8L

## Pin 1 (Reset):


The use of reset pin is to reset the ATmega8L microcontroller. This can be done by connecting this pin to ground. In normal mode of execution it should have at least 2.7V. Thus it is connected to +5 V through 10k ohm resistance .We should make sure that its potential be above 2.7 for proper execution of code.

## Pin 7 and 20 (Vcc):

Pin 7 and 20 should be connected to Power supply. (2.7 to 5.5 volt for ATmega8L)
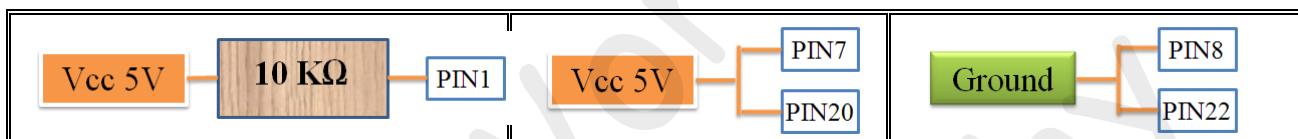
## Pin 8 and 22 (Ground):

Pin 8 and 22 should be connected to Ground. This ground should be common to for the entire circuit.



**Make sure Ground and Vcc do not get interchanged and Vcc should not exceed 5.5 V. If you connect supply wrongly, ATmega8L will suffer permanent damage.**

## Input and Output Ports

- In ATmega8L we have **three** I/O (input/output) ports viz. Port B, Port C and Port D.
- One can configure any pin of each of these ports as input or output pin by appropriate programming.

We will be using Port B pins (PB0 to PB3) as output pins because at pinPB1 and PB2 we have on-chip PWM output that can control the speed of motors.

Pin	PORT	Connection	PWM
14	PB0	Negative of right	NO
15	PB1	Positive of right	YES
16	PB2	Positive of Left	YES
17	PB3	Negative of Left	NO

Thus we can use Port C or Port D or remaining Pins of Port B as input. But for the sake of simplifying hardware connections **we choose Port D pins as input pins.**

## Burner (or programmer)

Burner (or programmer) is the circuit used to transfer the code from computer to microcontroller IC. For programming AVR there are different types of burners available Eg stk200, stk500, jtag2 etc.


We will be using **stk200** programmer.

### stk200 Programmer:

#### Requirements


- Parallel Port DB 25 connector (connects to the computer )
- 5 Pin RMC connector (connects to AVR PCB).
- 5 wired Bus

They are shown in following figure.

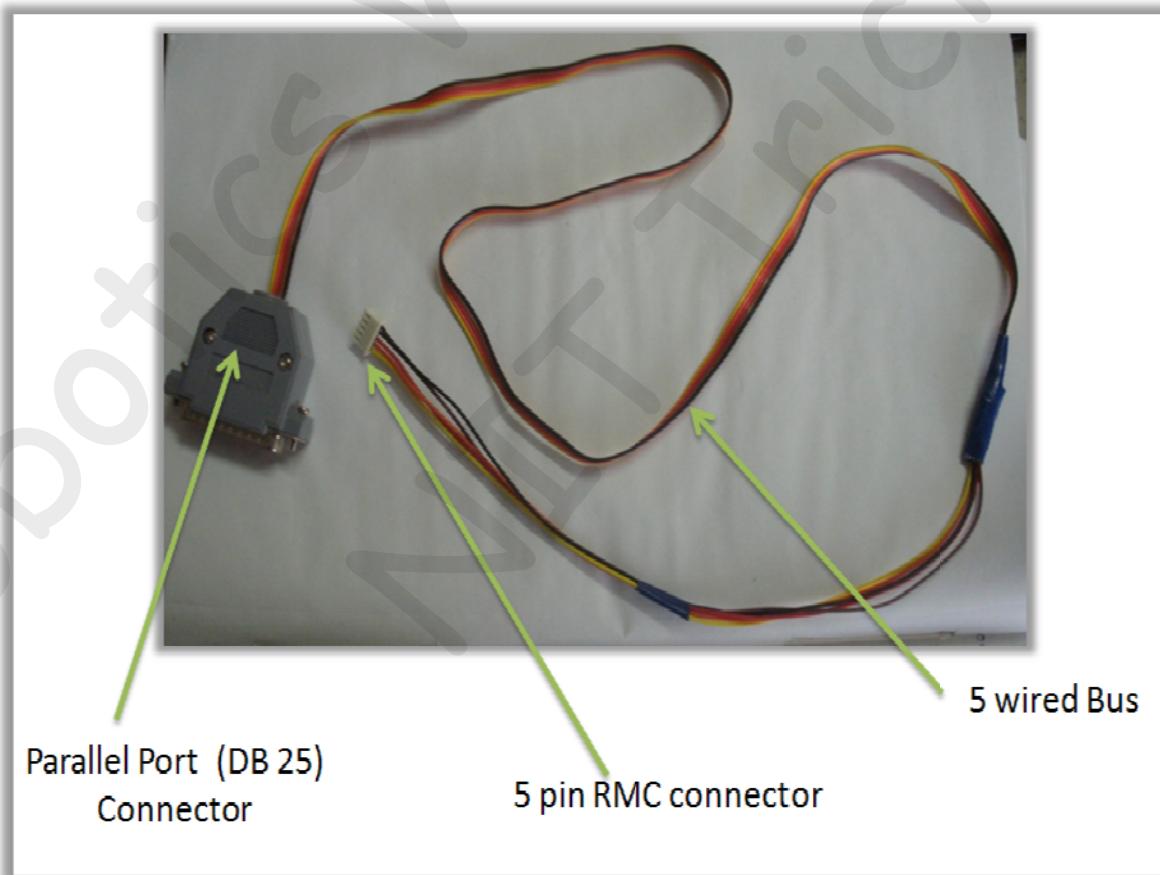
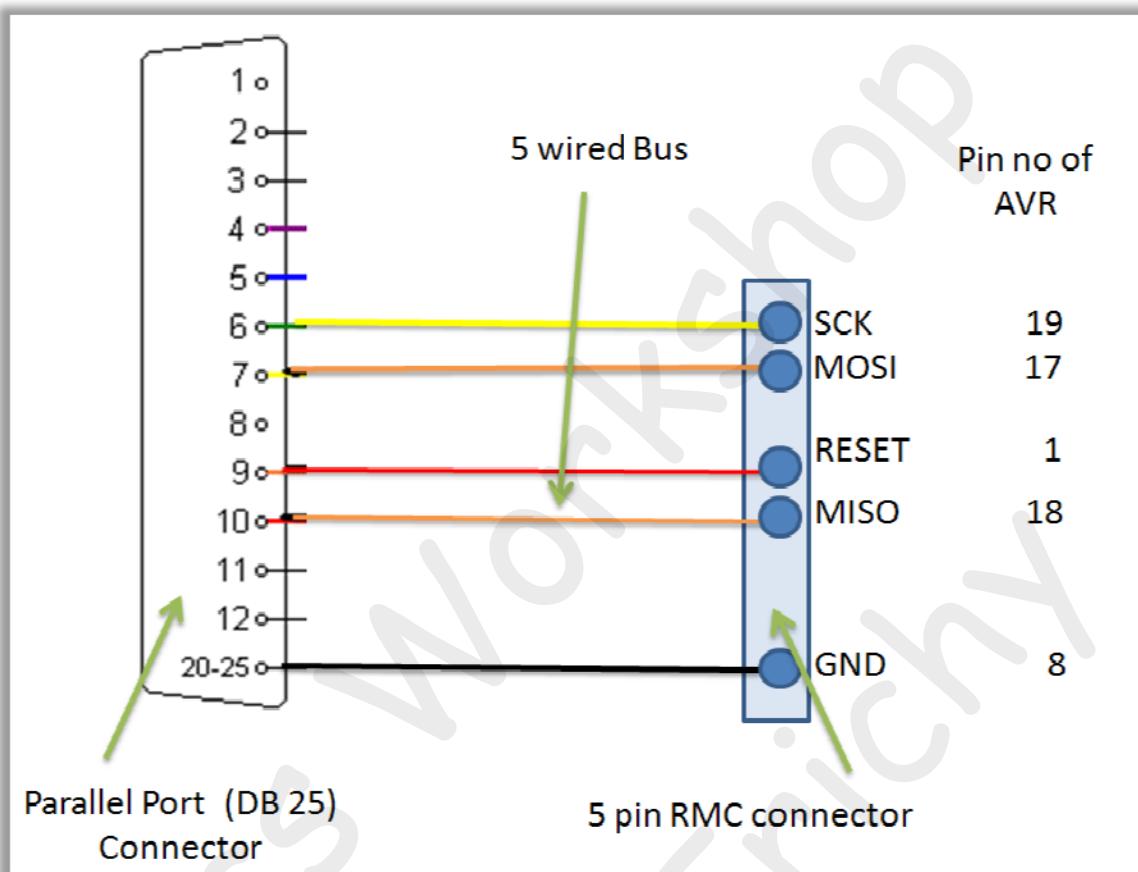
## Connections

Connections are given by the following figure.



## Explanations of Pins of ATmega8L

SCK	SPI Bus Master clock Input
MOSI	Master Output/Slave Input
RESET	Reset pin
MISO	Master Input/Slave Output
GND	Ground

## B) Software Details:

### Programming and Simulating

The program code acts as the decision-maker embedded in the microcontroller i.e. it decides what will be the outputs for particular set of input combination.

Programs for the AVR series of microcontrollers can be written in assembly (AVR ASM), C and BASIC. [AVR Studio](#), [WinAVR](#), etc. are some free development softwares for programming the AVR Microcontrollers. We will be using [winAVR](#) for programming and [AVR Studio](#) for simulating (*Simulation means debugging the code on software, one can virtually give the input and check the output for that code*).

In winAVR programmers Notepad we write our C code, after compilation it generates '[.hex](#)' file which is a hardware level code.

**Sample Code:** To blink a LED connected at pin 6 (PD4) of ATmega8L.

```
#include <avr/io.h> //header file to include input output port
#include <util/delay.h> //header file to include delay function
#define LED PD4

int main(void)
{
    DDRD = (1 << LED);
    /* DDR=Data Direction register... its to define PD4 OUTPUT pin
    rest bits of DDRD can be 0 or 1 does not make any significance */

    while (1)
    {
        PORTD = (1 << LED); // switch on
        _delay_ms(200);
        PORTD = (0 << LED); // switch off
        _delay_ms(200);
    }
    return 0;
}
```

# **MOTOR OUTPUT SYSTEM:**

For moving a robot we have two dc motors attached to wheels and gear system.

## **Why DC motors**

DC motors are most easy to control. One dc motor requires only two signals for its operation. If we want to change its direction just reverse the polarity of power supply across it. We can vary speed by varying the voltage across motor.

## **Use of gears**

The DC motors don't have enough torque to drive a robot directly by connecting wheels in it. Gears used to increase the torque of dc motor on the expense of its speed.

### **Mathematical interpretation:**

Rotational power (Pr) is given by:

$$Pr = \text{Torque} (T) * \text{Rotational Speed} (\omega)$$

Thus

$$T = \frac{Pr}{\omega}$$

Pr is constant for DC motor with constant input electrical power. Thus torque (T) is inversely proportional to speed ( $\omega$ ).

$$T \propto \frac{1}{\omega}$$

Thus to increase the value of torque we have to sacrifice speed.

### **Note:**

- In toy car, there is a gear box that contains several combinations of gears.
- Geared motor has a gear box at its front end.



Simple DC Motor of Toy Car



Gear Box of Toy Car



Geared DC Motor



Gear Box of Geared DC Motor

## Why two motors

By using two motors we can move the robot in any direction. This steering mechanism of robot is called **differential drive**.

Let's check how it works

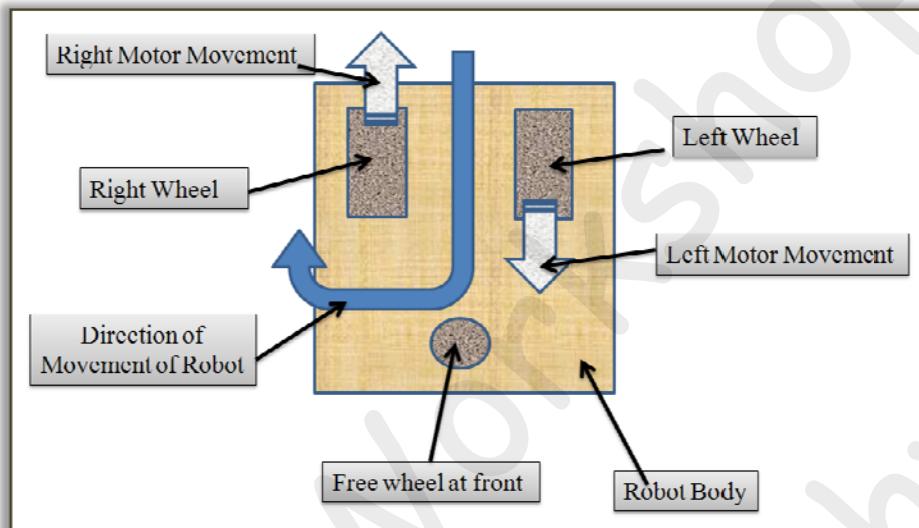


Figure. Description of various parts

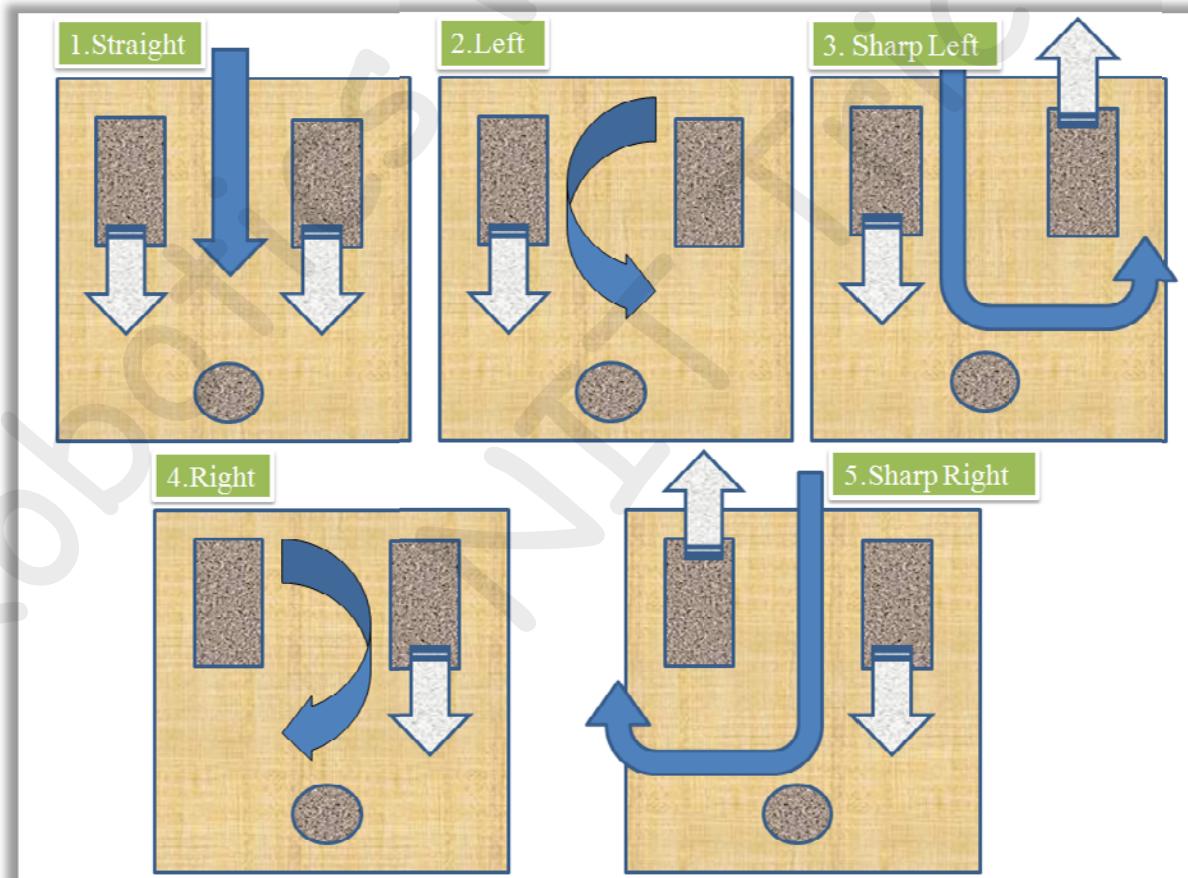


Figure. Movement of Robot

The table:

<b>Left Motor</b>	<b>Right Motor</b>	<b>Robot Movement</b>
Straight	Straight	Straight
Stop	Straight	Left
Reverse	Straight	Sharp left
Straight	Stop	Right
Straight	Reverse	Sharp Right
Reverse	Reverse	Reverse

## Use of Motor Driver

From microcontroller we can not connect a motor directly because microcontroller can not give sufficient current to drive the DC motors. *Motor driver is a current enhancing device; it can also act as a Switching Device.* Thus we insert motor driver between the motor and microcontroller.

Motor driver takes the input signals from microcontroller and generates corresponding output for motor.

### IC L293D

This is a motor driver IC that can drive two motor simultaneously. Let's see how we use this IC.

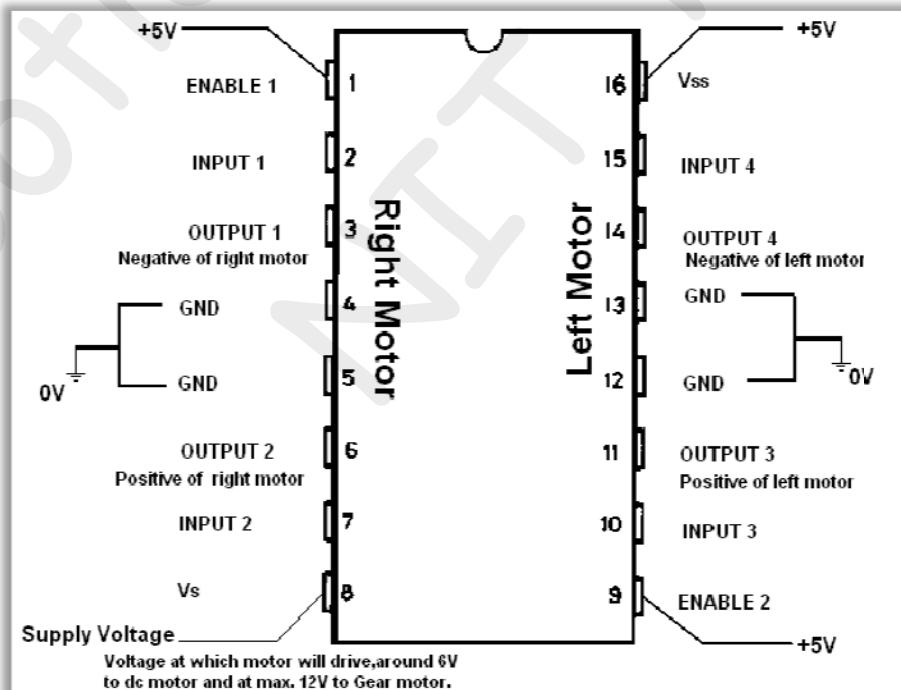


Figure. Pin Details of L293D

## Electrical Characteristics of L293D

Symbols	Parameter	Testing Condition	Min.	Max.	Units
Vss	Logic Supply Voltage Pin 16		4.5	36	V
Vs	Supply Voltage Pin 8		Vss	36	V
Ven L	Enable Low Voltage Pin 1 and 9		-0.3	1.5	V
Ven H	Enable High Voltage Pin 1 and 9	Vss<=7	2.3	Vss	V
		Vss>7	2.3	7	
VIL	Input Low Voltage Pin 2, 7, 10 and 15		-0.3	1.5	V
VIH	Input High Voltage Pin 2, 7, 10 and 15	Vss<=7	2.3	Vss	V
		Vss>7	2.3	7	

### Points regarding L293D

- ❖ Supply voltage (Vss) is the Voltage at which we wish to drive the motor. Generally we prefer 6V for dc motor and 6 to 12V for gear motor, depending upon the rating of the motor.
- ❖ Logical Supply Voltage will decide what value of input voltage should be considered as high or low .So if we set Logical Supply Voltage equal to +5V, then -0.3V to 1.5V will be considered as Input Low Voltage and 2.3 V to 5V will be considered as Input High Voltage.
- ❖ L293D has 2 Channels .*One channel is used for one motor.*
  - Channel 1 - Pin 1 to 8
  - Channel 2 - Pin 9 to 16
- ❖ Enable Pin is used to enable or to make a channel active. Enable pin is also called as Chip Inhibit Pin.
- ❖ All Inputs (Pin No. 2, 7,10and 15) to L293D IC are the respective outputs from microcontroller (ATmega8L).
 


E.g.-*We connected Pin No. 2, 7, 10 and 15 of L293D IC to Pin No. 14, 15,16and 17 of ATmega8L respectively in our robots, because on pin 15 and 16 of ATmega8L we can generate PWM.*
- ❖ All Outputs (Pin No. 3, 6,11and 14) of L293D IC goes to the inputs of Right and Left motors.

### Output Connections

- OUTPUT 1 (Pin No 3) --- Negative Terminal of Right Motor
- OUTPUT 2 (Pin No 6) --- Positive Terminal of Right Motor
- OUTPUT 3 (Pin No 10) --- Positive Terminal of Left Motor
- OUTPUT 4 (Pin No 14) --- Negative Terminal of Left Motor

For one motor:

Positive Terminal	Negative Terminal	Motor Output
0	0	No movement
Vss	0	Straight
0	Vss	Reverse
Vss	Vss	No Movement

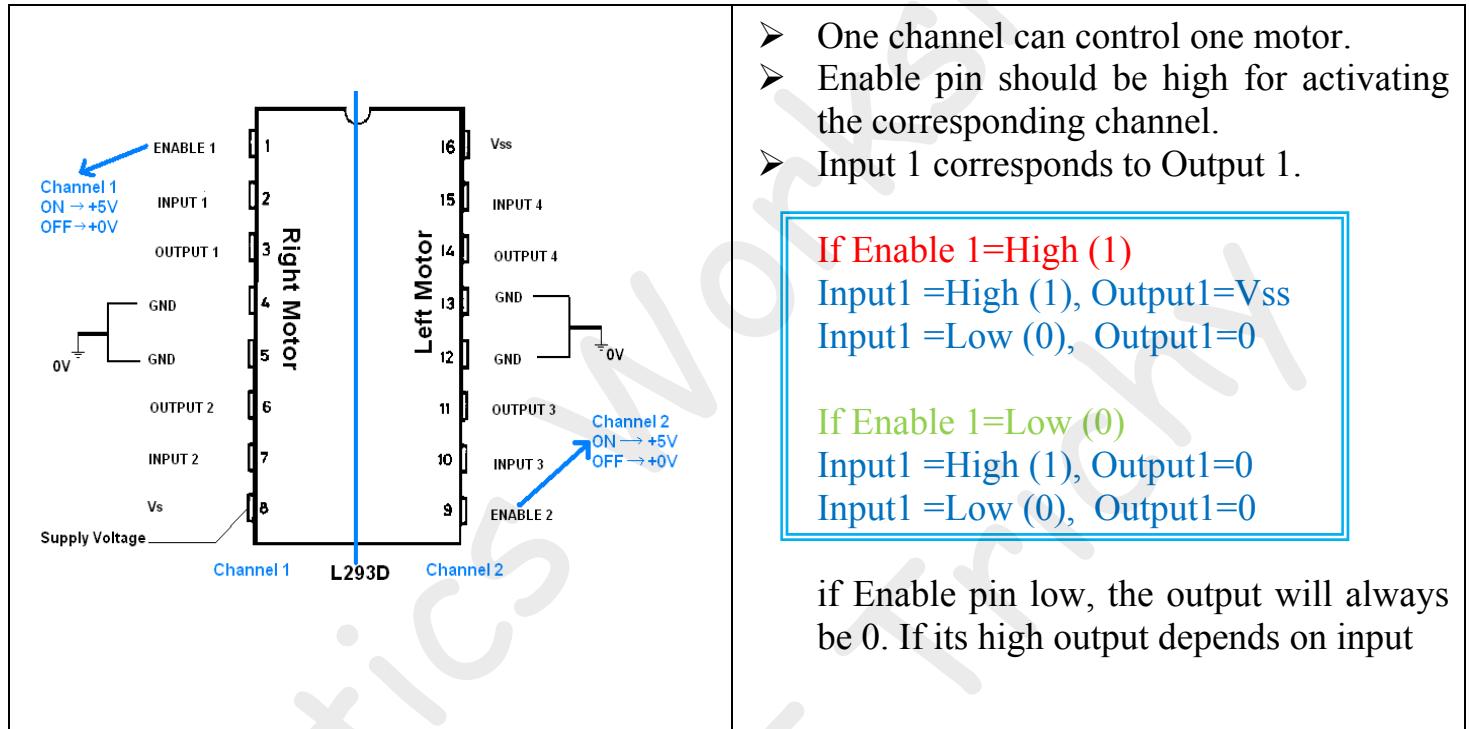

Let's check the sample outputs for some sample inputs (when both the Enable pins are high):

Input 1	Input 2	Input 3	Input 4	Output 1	Output 2	Output 3	Output 4	Motors Output		Movement
								Right	Left	
Low	High	High	Low	0	Vss	Vss	0	Straight	Straight	Straight
Low	High	Low	Low	0	Vss	0	0	Straight	No mov	Left Turn
Low	Low	High	Low	0	0	Vss	0	No mov	Straight	Right Turn
Low	High	Low	High	0	Vss	0	Vss	Straight	Reverse	Sharp Left
High	Low	High	Low	Vss	0	Vss	0	Reverse	Straight	Sharp Right
High	Low	Low	High	Vss	0	0	Vss	Reverse	Reverse	Backward

You can see the datasheet of that IC for more details.

## **Algorithm for Line Follower**

There are various line follower algorithms. The main use of the algorithm is to move the robot on the line in a smooth fashion. Apart from the task, the algorithm also depends on hardware including number of sensors, type of motors, chassis etc.

Same problem can be approached by different algorithms. Readers are encouraged to develop their own algorithms.

## Appendix:

### 1. Printed Circuit Board

When making the circuit with the electronic parts of the resistors, the capacitors, the transistors, the ICs and so on, it is necessary to connect the lead line of each part appropriately. Also, each part must be fixed, too. The printed circuit board is used to do the wiring among the parts and the fixation of the part.

#### Advantages:

- Reliability and durability due to compact nature of the circuit especially needed for mobile applications like robotics.
- Easy debugging.
- Large number of circuits can be made with a greater accuracy and at a cheap cost.
- Chances of loose connections get eliminated.

#### Disadvantages

- Once the circuit is made on a PCB its layout cannot be changed.
- PCB leads can burn at higher values of current rendering it useless for further use
- PCB designing can be a tedious and time consuming process.

## PCB layout that will be given in Workshop

Bottom View:

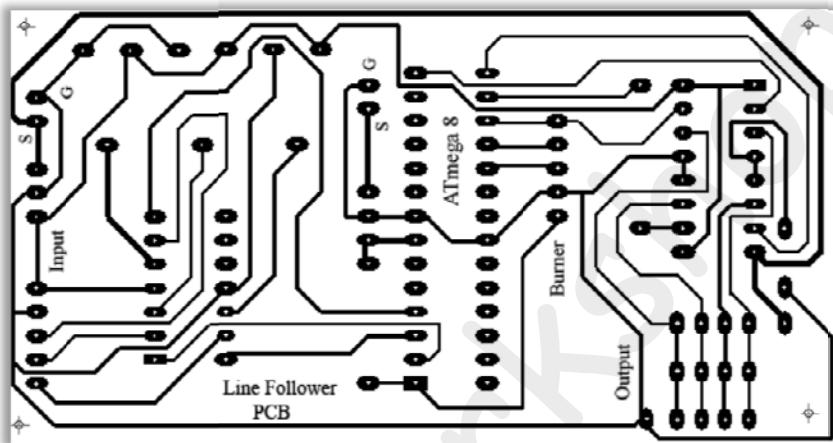


Figure: PCB Layout designed by Software

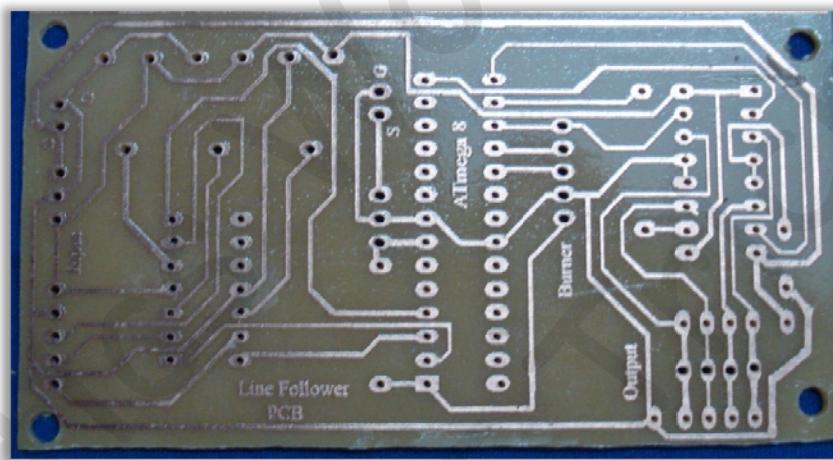


Figure: Photo

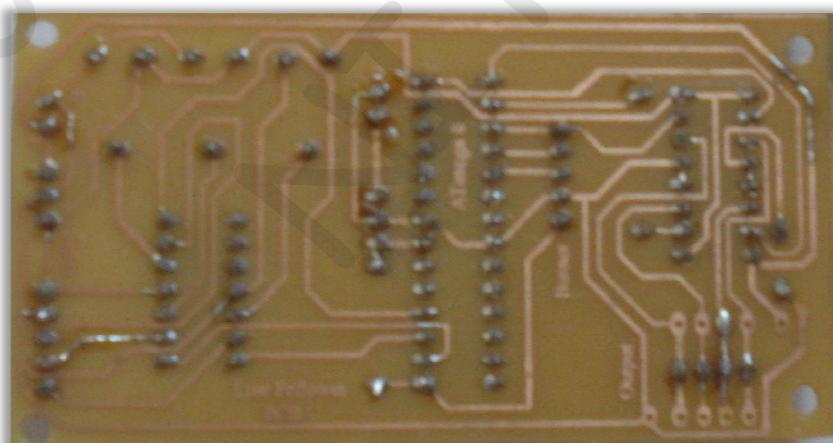


Figure: After Soldering

Top View:

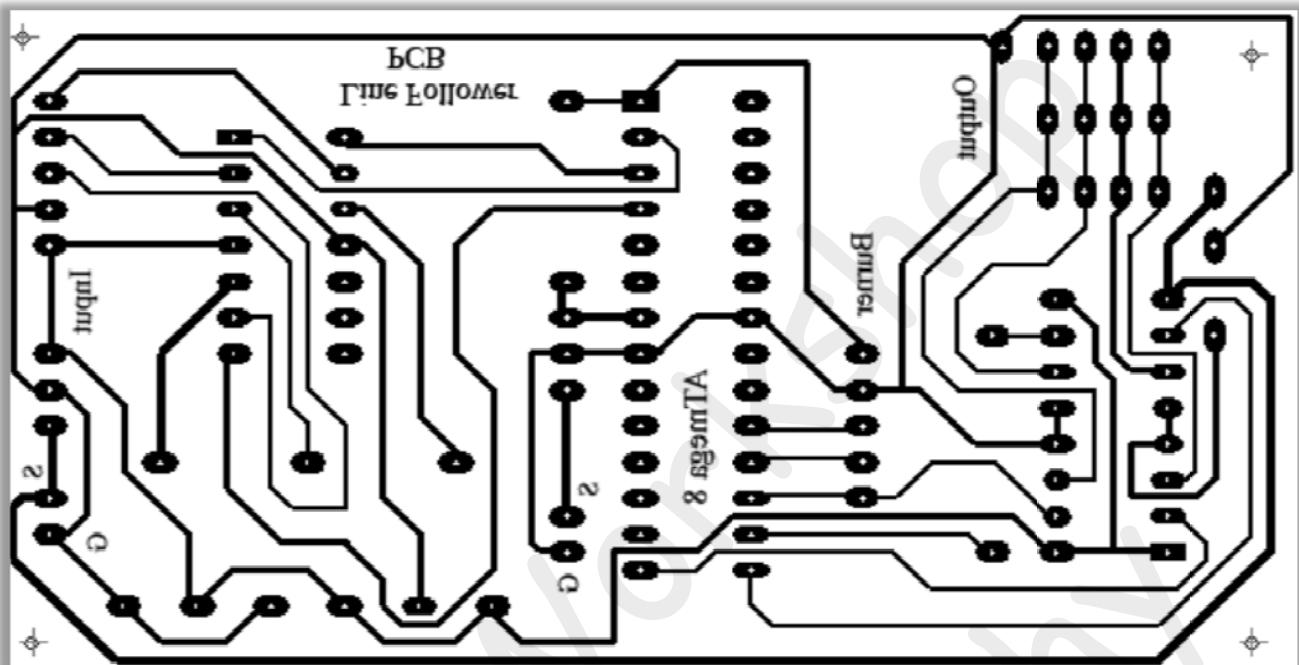


Figure: Mirror image of Bottom Layout


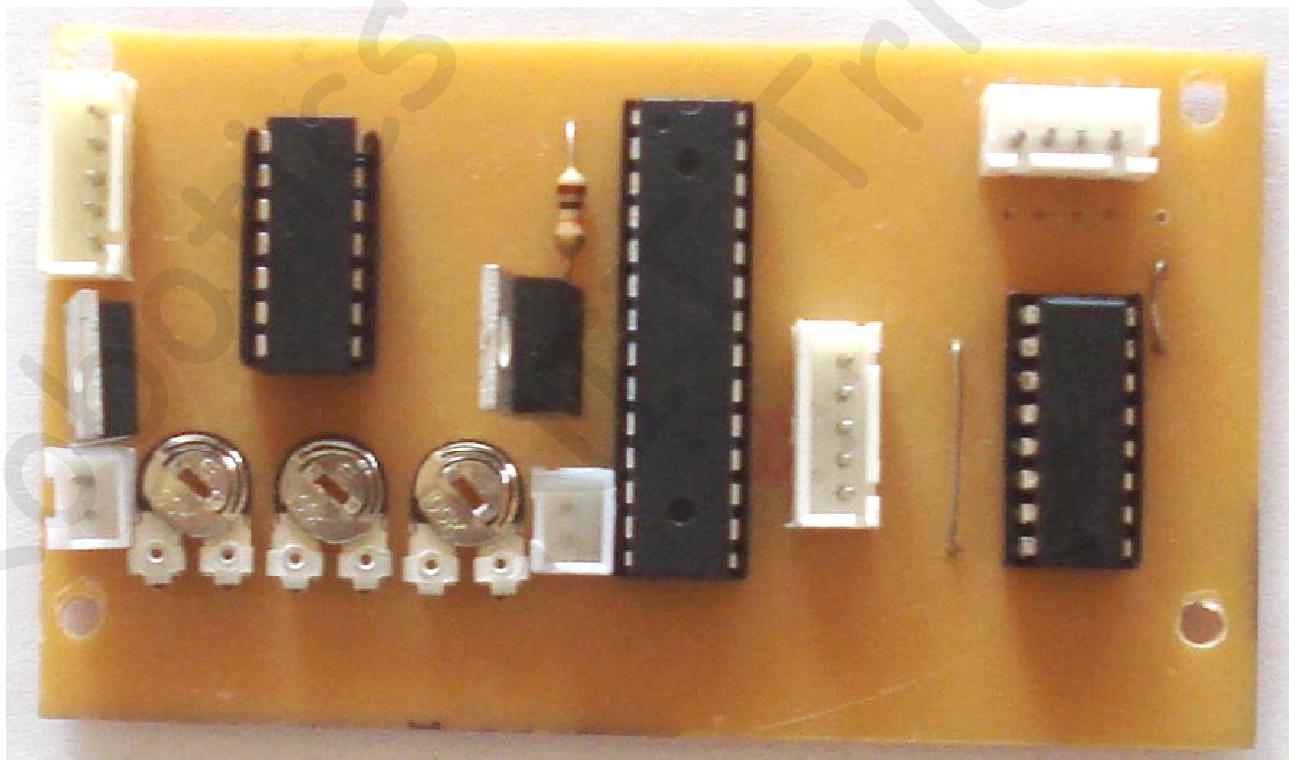
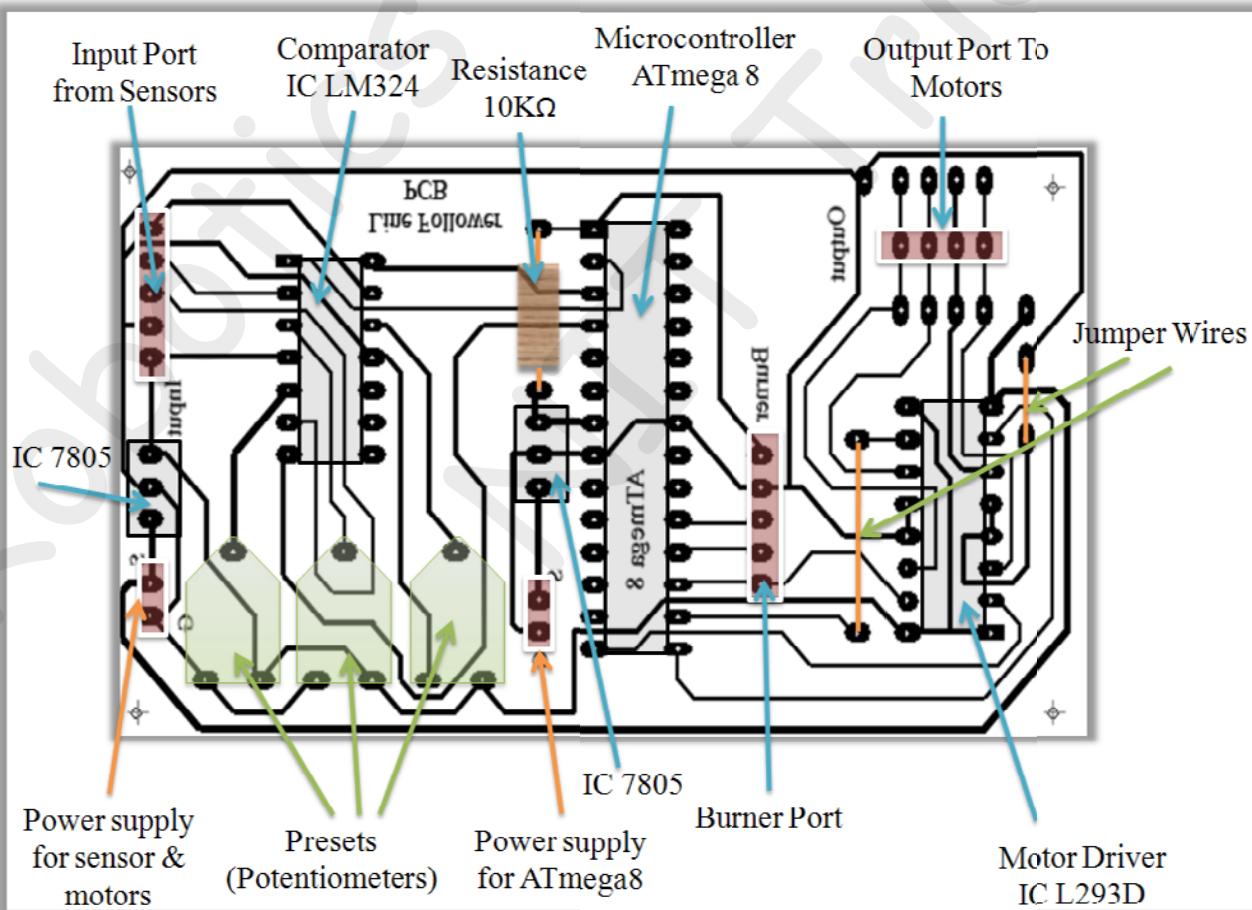



Figure: After placing all Components

## Explanation of all components:

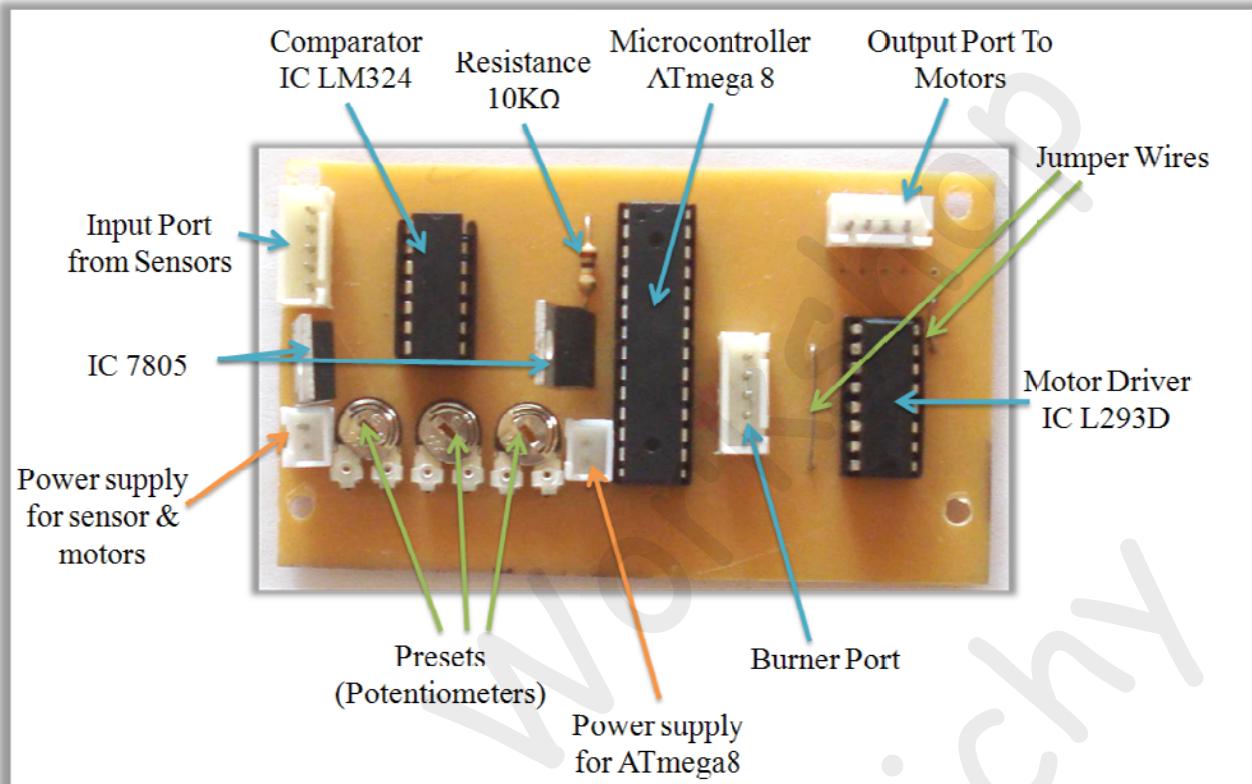

1) Sensor PCB


**Bottom Layout:**

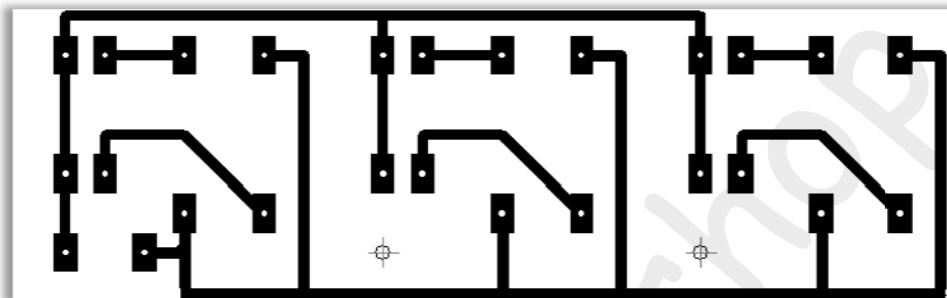


2) **Bottom View:**



3) **Top View:**

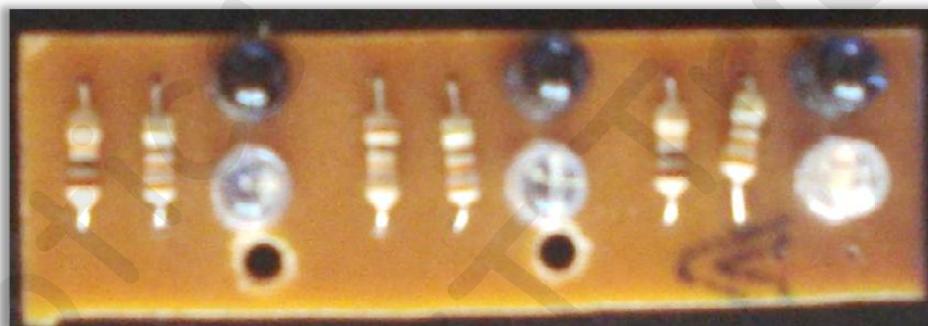


**Explanation:**

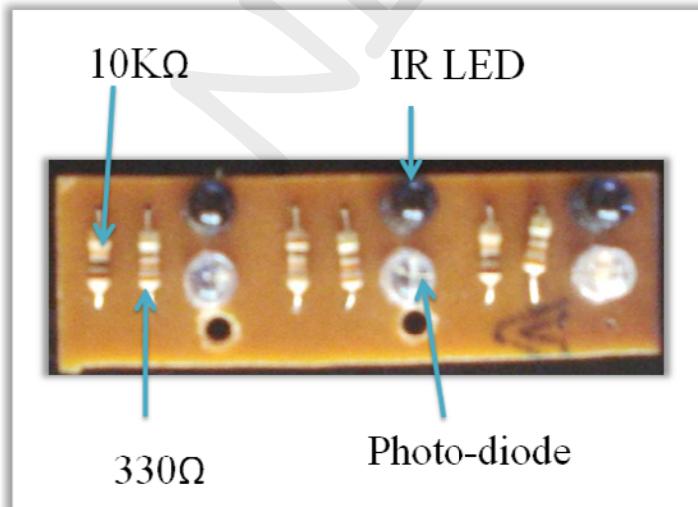
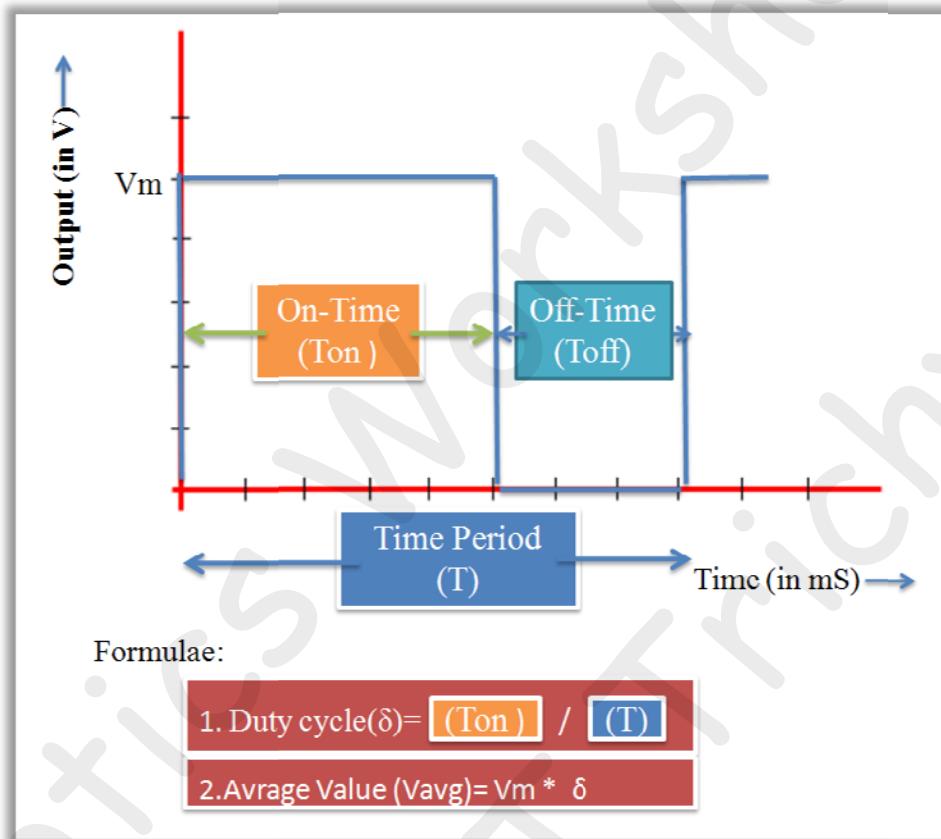
# PWM

**Pulse Width Modulation (PWM)** is a method to generate **Periodic Square Wave** of various frequencies (time period) or duty-cycles.

The periodic square wave has two levels (high or low), with some constant frequency and duty-cycle.




## Definitions:

From above figure we can define some terms.

- **Time period (T):** The minimum time after which function repeats itself is called as Time period.
- **Frequency (f):**  $=1/T$
- **On Time (Ton):** Time for which function is at high voltage.
- **Off Time (Toff):**  $= T - Ton$
- **Duty Cycle ( $\delta$ ):**  $=(Ton)/T$
- **Average Value( $V_{avg}$ ):**  $=V_m * \delta$   
( $V_m$  is value of high voltage)

## Examples

Example 1:

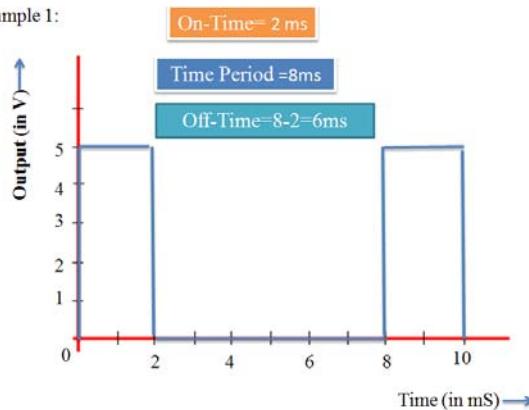


Calculations:

$$\delta = (2 \text{ ms} / 8 \text{ mS}) = 0.25 \text{ (or } 25\%)$$

$$V_{avg} = 5 * \delta = 5 * 0.25 = 1.25 \text{ V}$$

Example 2:

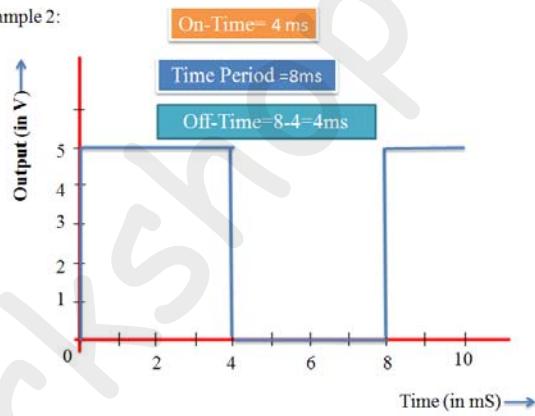


Calculations:

$$\delta = (4 \text{ ms} / 8 \text{ mS}) = 0.5 \text{ (or } 50\%)$$

$$V_{avg} = 5 * \delta = 5 * 0.5 = 2.5 \text{ V}$$

Example 3:

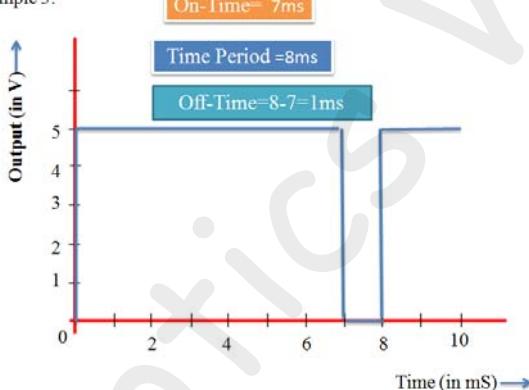


Calculations:

$$\delta = (7 \text{ ms} / 8 \text{ mS}) = 0.875 \text{ (or } 87.5\%)$$

$$V_{avg} = 5 * \delta = 5 * 0.875 = 4.375 \text{ V}$$

Example 4:

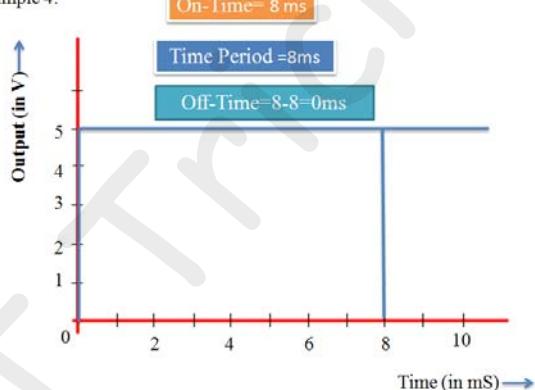


Calculations:

$$\delta = (8 \text{ ms} / 8 \text{ mS}) = 1 \text{ (or } 100\%)$$

$$V_{avg} = 5 * \delta = 5 * 1 = 5 \text{ V}$$
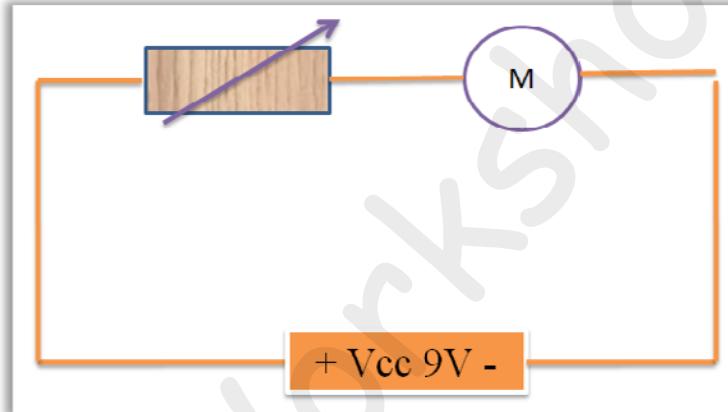
## USE of PWM in DC Motor

For example: If a person wants to drive a DC motor with variable speed but he only has **constant Voltage** supply. As an alternative for PWM he can add a variable resistance in series with the motor (As shown in figure).




The drawbacks of this connection are:

1. The resistance value cannot be varied dynamically (automation is difficult).
2. There will be unnecessary power loss across the resistor.

Now “By adjusting the duty cycle of the signal (modulating the width of the pulse, hence the 'PWM') i.e., the time fraction for which it is "on", the average power can be varied, and hence the motor speed.”

In other words by varying the duty cycle we are getting different values of average voltage ( $V_{avg}$ ) across the motor resulting in different speeds.

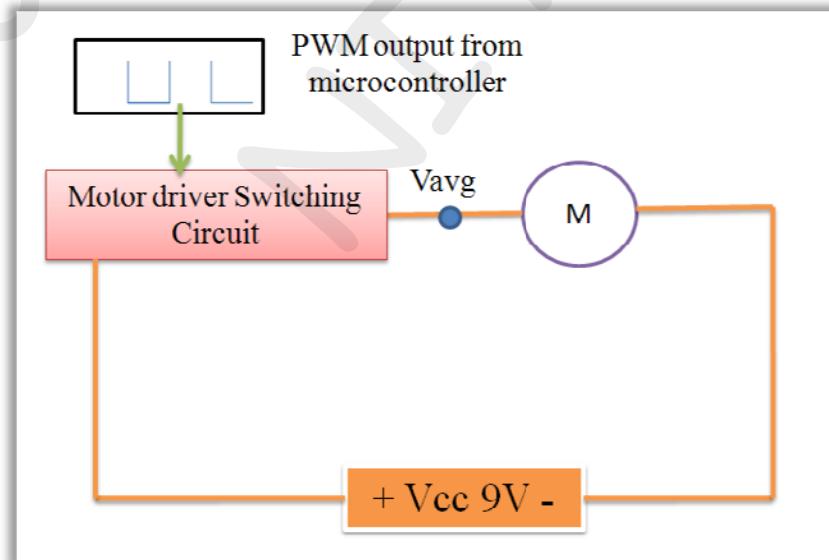We can design the system as shown in the following figure:



Now

$$V_{avg} \propto \delta$$

And

$$\text{DC Motor Speed} \propto V_{avg}$$

Thus

$$\text{DC Motor Speed} \propto \delta$$

### Advantages of PWM:

1. Here the switch is either on or off unlike normal regulation(using variable resistance), so less power is wasted as heat and smaller heat-sinks can be used.
2. Since no resistor is used, there is no power loss.
3. Can be easily automated by programmable control.

### Disadvantages:

1. We require extra circuitry to implement PWM (in AVR we have in built PWM-circuitry on chip).
2. Some authorities claim the pulsed power puts more stress on the DC motor bearings and windings, shortening its life.

### Implementation of PWM:

For developing PWM, we require two properties:

1. Time Period (T)
2. On-Time Period ( $T_{on}$ )

### Implementation of PWM in microcontroller:

In microcontroller we use clock of several Mega Hz. Thus time of one clock

$$T_{clk} = 1/(\text{clock frequency})$$

E.g. In ATmega 8 clock frequency is approximately 1 Mega Hz.

$$T_{clk} = 1/(1\text{M Hz}) = 1 \mu\text{s}$$

For implementation of PWM in microcontroller we require these variables:

- ❖  $Nt$ = Number of clock cycles for one time period of PWM

$$Nt = T / T_{clk}$$

- ❖  $OCR$ = Number of clock cycles for On Time of PWM

$$OCR = T_{on} / T_{clk}$$

- ❖  $Ni$ = It is a index of counter, that counts from  $Nt$  to zero and Zero to  $Nt$  in each cycle.

When if  $Ni \geq OCR$  then **PWM Output=Low**  
And if  $Ni < OCR$  then **PWM Output=High**

